

QUIZ – ANSWER KEY

QUIZ NO: 111

TOPIC: ELECTRICAL ENGINEERING

DATE: 05/10/2022

1. The condition for maximum voltage to be transferred to the load is?

- [A] Source resistance greater than load resistance
- [B] Source resistance less than load resistance
- [C] Source resistance equal to load resistance
- [D] Source resistance greater than or equal to load resistance

Answer: B

2. The condition for maximum current to be transferred to the load is?

- [A] Source resistance greater than or equal to load resistance
- [B] Source resistance equal to load resistance
- [C] Source resistance less than load resistance
- [D] Source resistance greater than load resistance

Answer: D

3. The condition for maximum power to be transferred to the load is?

- [A] Source resistance equal to load resistance
- [B] Source resistance greater than load resistance
- [C] Source resistance greater than or equal to load resistance

[Join our social media](#)



QUIZ – ANSWER KEY

[D] Source resistance less than load resistance

Answer: A

4. After how many time constants, the transient part reaches more than 99 percent of its final value?

[A] 2

[B] 3

[C] 4

[D] 5

Answer: D

5. The value of the time constant in the R-L circuit is?

[A] L/R

[B] R/L

[C] R

[D] L

Answer: A

6. The circuit is said to be in resonance if the current is _____ with the applied voltage ?

[A] in phase

[B] out of phase

[C] 45° out of phase

[D] 90° out of phase

Answer: A

Join our social media



QUIZ – ANSWER KEY

7. As $X_L = X_C$ in a series resonance circuit, the impedance is _____ ?
- [A] purely capacitive
 - [B] purely inductive
 - [C] purely resistive
 - [D] capacitive and inductive

Answer: C

8. The voltage across the LC combination in a series RLC circuit is?
- [A] 0
 - [B] 1
 - [C] 2
 - [D] 3

Answer: A

9. Determine the current if a 20 coulomb charge passes a point in 0.25 seconds ?
- [A] 10 A
 - [B] 20 A
 - [C] 2 A
 - [D] 80 A

Answer: D

10. The current law represents a mathematical statement of fact that _____ ?
- [A] voltage cannot accumulate at node
 - [B] charge cannot accumulate at node
 - [C] charge at the node is infinite
 - [D] none of the mentioned

Answer: B

Join our social media

